

# Important RF Components

## Contributed to the ACAS 2016 School

John D. Fox

Applied Physics Department  
Stanford University

Stanford Linear Accelerator Center


Work supported by the DOE under contract # DE-AC02-76SF00515 and the DOE LHC  
Accelerator Research Program LARP

January 2016

# Outline

- 1 Power Splitters and Combiners
- 2 Hybrid Junctions
- 3 Directional Couplers
- 4 Circulators
- 5 Acknowledgements


## 2 Way, or N Way, power splitters and Combiners

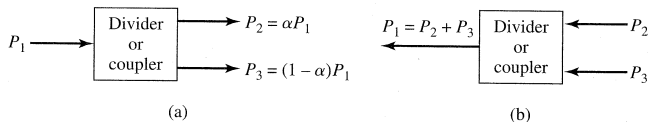

**FIGURE 7.1** Power division and combining. (a) Power division. (b) Power combining

- Preserve Characteristic Impedance at each port
- What does a BNC T do?


# Resistive Splitter

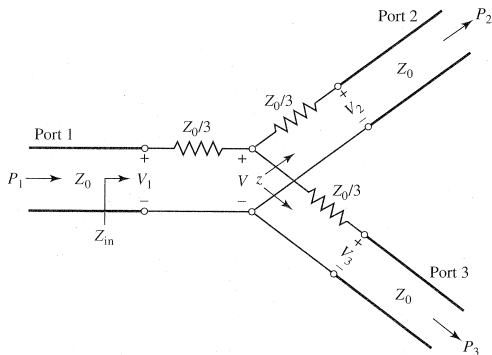

**FIGURE 7.7** An equal-split three-port resistive power divider.

- Preserves Characteristic Impedance at each port
- Does it have any isolation?
- Does it have losses?

# Wilkinson Power divider

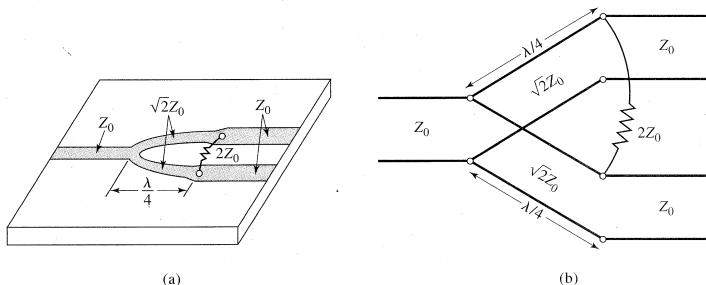

**FIGURE 7.8** The Wilkinson power divider. (a) An equal-split Wilkinson power divider in microstrip form. (b) Equivalent transmission line circuit.

- Preserve Characteristic Impedance at each port
- Does it have losses?
- What signals go in the internal load?

# Buy a 2 Way broadband

## Merrimac

- Bandwidths to 0.5 to 18.0 GHz
- Excellent Phase and Amplitude Balance
- High Isolation between Output Ports

### PDM-02S series

0° POWER DIVIDER/COMBINERS, SMA  
Two Way, Multi-Octave, Stripline



4.25

These multi-section devices are designed to provide precise in-phase division of microwave signals in three multi-octave bands up to 0.5 to 18.0 GHz. It is one of many Power Dividers developed to meet broadband ECM requirements with very tight amplitude and phase balance, and high output port isolation.


These complex designs have been developed using original analysis of stripline theory on the in-house CAD/CAM. Design variations can be realized by recalling critical parameters, which can then be readily modified for specific requirements with artwork and machining drawings being produced directly.

All MERRIMAC stripline products are designed for exceptional reliability and rigorous environments such as in uninhabited airborne specifications. Each may be supplied screened to meet specific military and space applications.

Model Number	Frequency Range GHz	Output Isolation min.	Insertion Loss max.	Phase Balance Max.	Amplitude Balance Typ.	VSWR max. In/Out	Max. Average Power with Load	Average VSWR of
PDM-02S-4G	0.5 to 8.0	19 dB	0.9 dB	4°	0.3 dB	1.30:1	30 W 10 W 1 W	2.0:1
PDM-02S-6G	1.0 to 12.4	15 dB	1.6 dB	6°	0.3 dB	1.65:1	30 W 10 W 1 W	
PDM-02S-9G	1.5 to 18.0	18 dB	1.5 dB	8°	0.4 dB	1.35:1	30 W 10 W 1 W	

Advanced Specifications

#### Package Outline

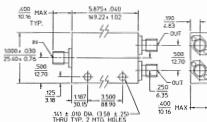


#### COMMON SPECIFICATIONS

RF Impedance: 50 Ω nom.  
Operating Temperature: -55° to +85°C  
Connectors: SMA Female to meet interface requirements of MIL-C-39012  
Weight, nominal: 3.5 oz (100 g)

#### AVAILABLE SPECIFICATIONS

Similar stripline designs of Power Dividers up to 16 ways, and for frequencies to 20 GHz are available as both custom and catalog products.


# Hybrids of 2, 4 or N ports

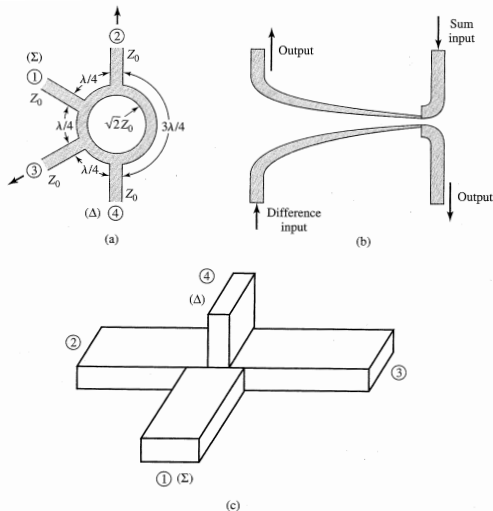

**FIGURE 7.43**

Hybrid junctions. (a) A ring hybrid, or *rat-race*, in microstrip or stripline form. (b) A tapered coupled line hybrid. (c) A waveguide hybrid junction, or *magic-T*.
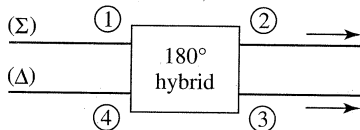
## 2 way 180 degree $\Delta\Sigma$ hybrid




Symbol for a 180° hybrid junction.

$$[S] = \frac{-j}{\sqrt{2}} \begin{bmatrix} 0 & 1 & 1 & 0 \\ 1 & 0 & 0 & -1 \\ 1 & 0 & 0 & 1 \\ 0 & -1 & 1 & 0 \end{bmatrix}.$$


- Preserve Characteristic Impedance at each port
- Does it have losses?
- Can it Add and Subtract?



# 90 Degree Hybrid

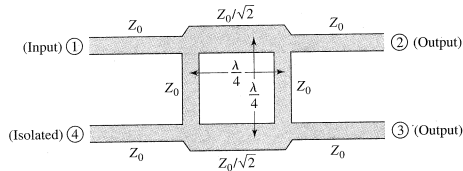

**FIGURE 7.21** Geometry of a branch-line coupler.

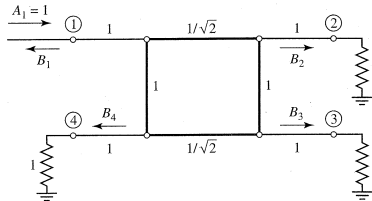


**FIGURE 7.22** Circuit of the branch-line hybrid coupler in normalized form.

- What Bandwidth does this work over?
- Does it have losses?
- What signals go to port 4??

# 90 Degree Hybrid

## 7.5 The Quadrature (90°) Hybrid

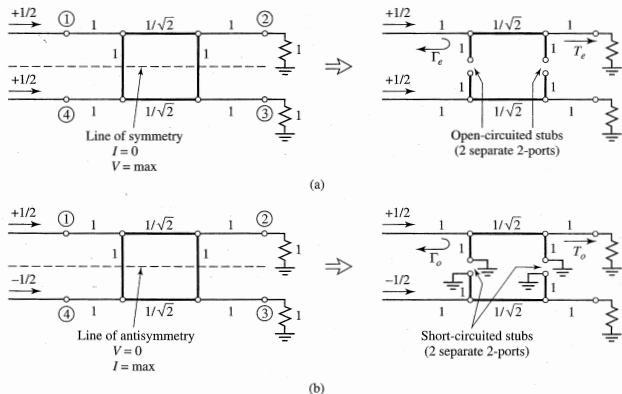

**FIGURE 7.23** Decomposition of the branch-line coupler into even- and odd-mode excitations


- What Bandwidth does this work over?
- Does it have losses?
- What signals go to port 4?

# Buy a 90 Degree Hybrid


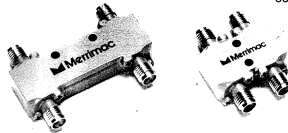
## QHM-2M/QHM-3M series

90° POWER DIVIDER/COMBINER, SMA  
Low Cost, Stripline Hybrid Couplers



- 500 MHz to 18 GHz Frequency Range
- Octave and Multi-Octave Models
- Low Insertion Loss and VSWR


Model Number	Frequency Range, GHz	*Coupling Loss, dB	Frequency Sensitivity	Isolation dB min.	Power Avg. Peak	VSWR max	Weight oz.(g)	Outlin Ref
QHM-2M-.75G	0.5 - 1.0	3.1 ± 0.6	± 0.5 dB	28	50 W 3 kW	1.10:1	1.2 (34)	4
QHM-2M-1.5G	1.0 - 2.0	3.1 ± 0.6	± 0.5 dB	28	50 W 3 kW	1.10:1	0.85 (24)	5
QHM-2M-3G	2.0 - 4.0	3.1 ± 0.6	± 0.5 dB	22	50 W 3 kW	1.20:1	0.65 (18)	1
QHM-2M-4G	2.6 - 5.2	3.1 ± 0.6	± 0.5 dB	20	50 W 3 kW	1.25:1	0.60 (17)	2
QHM-2M-6G	4.0 - 8.0	3.2 ± 0.7	± 0.5 dB	18	50 W 3 kW	1.25:1	0.60 (17)	2
QHM-2M-9G	6.0 - 12.4	3.2 ± 0.7	± 0.5 dB	18	50 W 3 kW	1.30:1	0.60 (17)	2
QHM-2M-12G	7.5 - 16.0	3.4 ± 0.9	± 0.6 dB	15	50 W 2 kW	1.40:1	0.65 (18)	3
QHM-2M-15G	12 - 18.0	3.4 ± 1.0	± 0.7 dB	15	50 W 1 kW	1.40:1	0.65 (18)	3
QHM-3M-5G	2.0 - 8.0	3.3 ± 0.8	± 0.4 dB	17	30 W 3 kW	1.30:1	1.65 (46)	6
QHM-3M-8G	4.0 - 12.4	3.3 ± 0.8	± 0.4 dB	17	20 W 2 kW	1.35:1	1.1 (30)	7

\*Coupling Loss includes Insertion Loss and Frequency Sensitivity

### Package Outline

OUTLINE	A	B	C	D	E	WT. OZ. (G)
1	1.60 29.27	.500 12.70	.315 7.98	.500 12.70	.640 16.26	.63 (18)
2	1.00 25.40	.500 12.70	.315 7.98	.500 12.70	.560 14.17	.60 (17)
3	1.00 25.40	.500 12.70	.315 7.98	.500 12.70	.560 14.17	.63 (18)

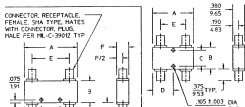
CONNECTOR, RECEPTACLE,  
FEMALE, SMA TYPE, MATES  
WITH CONNECTOR, PLUG,  
MALE PER MIL-C-39012 TYP.



The octave band QHM-2M series and multi-octave QHM-3M series of Hybrid Couplers have been designed using miniaturized stripline construction to achieve high isolation and low VSWR. They may be used in a wide variety of applications requiring equal division of power or combination of signals 90° out of phase, such as in mixers, modulators and phase shifters.

MERRIMAC Hybrid Couplers are designed to meet the requirements of MIL-P-23971, and may be ordered in accordance to this and other similar specifications. All units are available screened for use in space and harsh environments, where reliability is critical.


# Directional Coupler

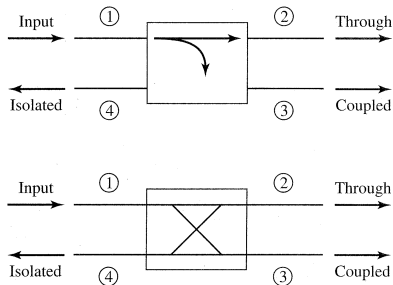


**FIGURE 7.4** Two commonly used symbols for directional couplers, and power flow conventions.

- What Bandwidth does this work over?
- Does it have losses?
- What happens if you drive port 3?

# Even/Odd Analysis of the two port coupler

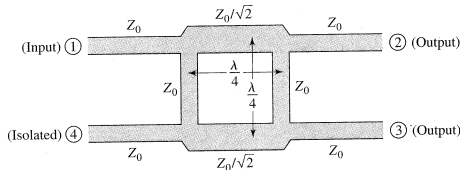


**FIGURE 7.21** Geometry of a branch-line coupler.

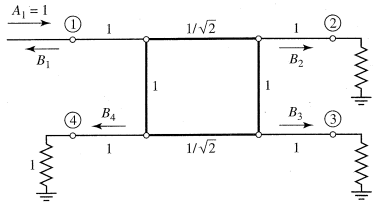

**FIGURE 7.22** Circuit of the branch-line hybrid coupler in normalized form.

- What Bandwidth does this work over?
- Does it have losses?
- What signals go to port 4??


# Microstrip Directional Coupler

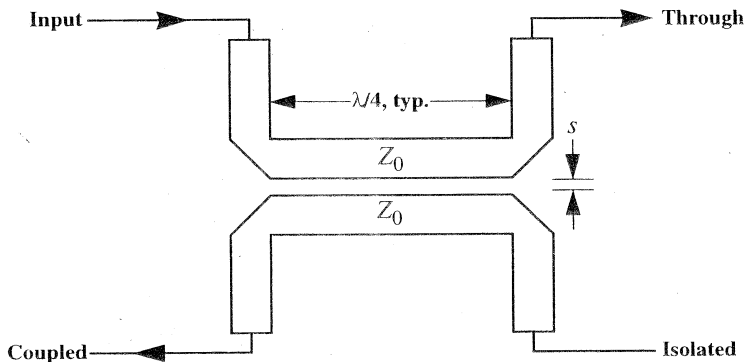


**FIGURE 7.46.** Classical microstrip directional coupler

- What Bandwidth does this work over?
- Does it have losses?
- What determines the coupling strength?

# Bethe-Style Waveguide Coupler

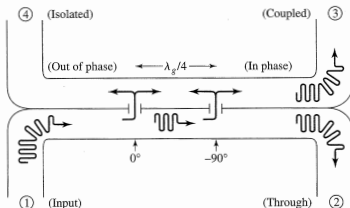

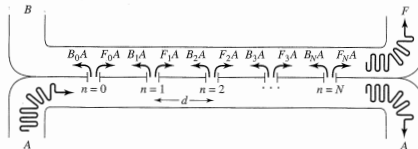Basic operation of a two-hole directional coupler.




7.19 Geometry of an  $N + 1$  hole waveguide directional coupler.

- What Bandwidth does this work over?
- What is the advantage of lots of holes?

# Circulators

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{12} & 0 & S_{23} \\ S_{13} & S_{23} & S_{33} \end{bmatrix}. \quad 7.7$$

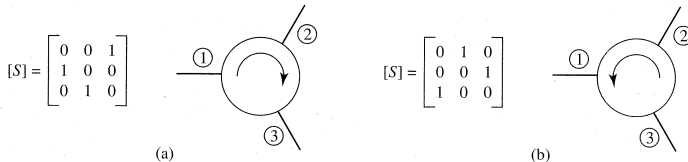

**FIGURE 7.2** The two types of circulators and their  $[S]$  matrices. (The phase references for the ports are arbitrary.) (a) Clockwise circulation. (b) Counterclockwise circulation.

- What Bandwidth does this work over?
- Does it have losses?
- How does this work?



# An Example - the Telephone Hybrid

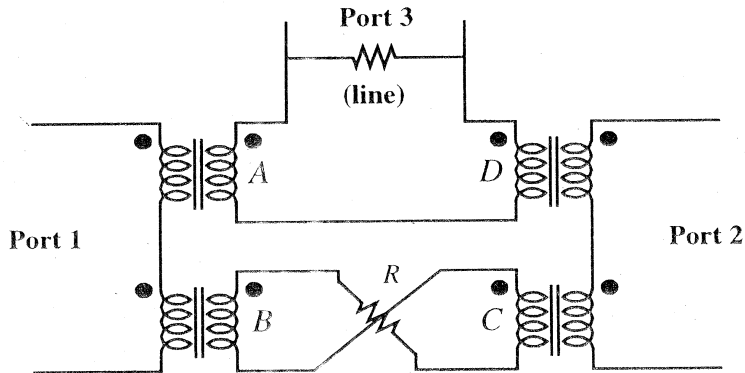


FIGURE 7.31. Classic telephone hybrid<sup>30</sup>

- Why do you want this in a telephone?
- What signals go on each port?

# Giving Credit, where Credit is Due

- Thanks to David Pozar, *Microwave Engineering*
- Thanks to Tom Lee *Planar Microwave Engineering*
- For the use of their figures in this talk
- Both have excellent books
- Thanks to Merrimac Corporation for the old catalog figures