

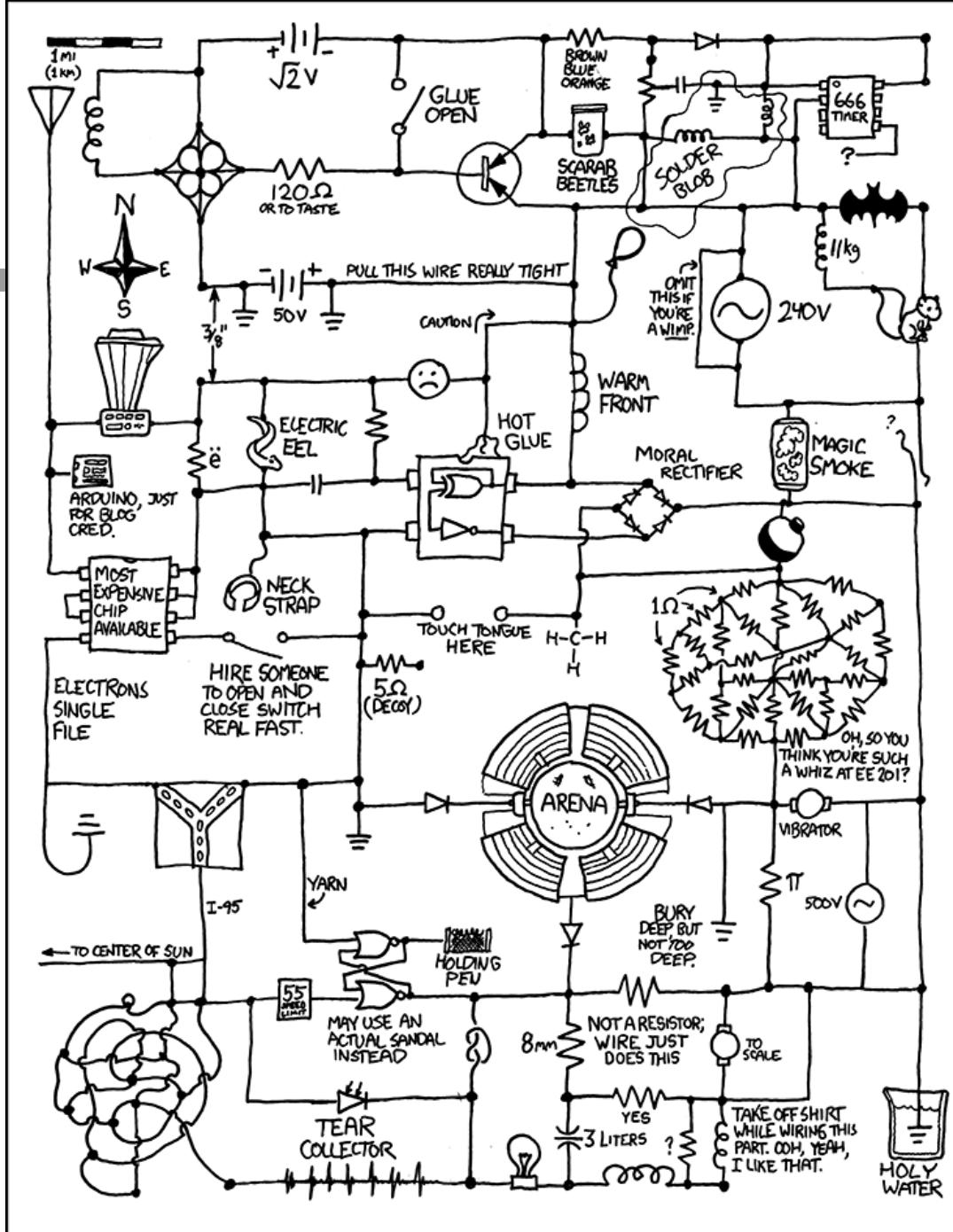
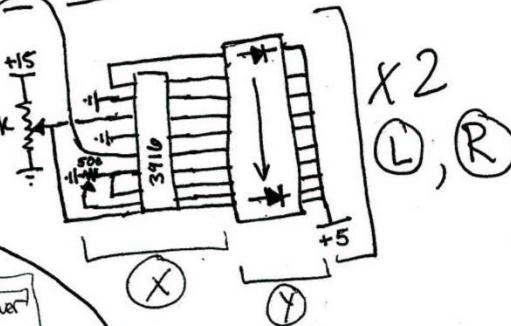



XKCD

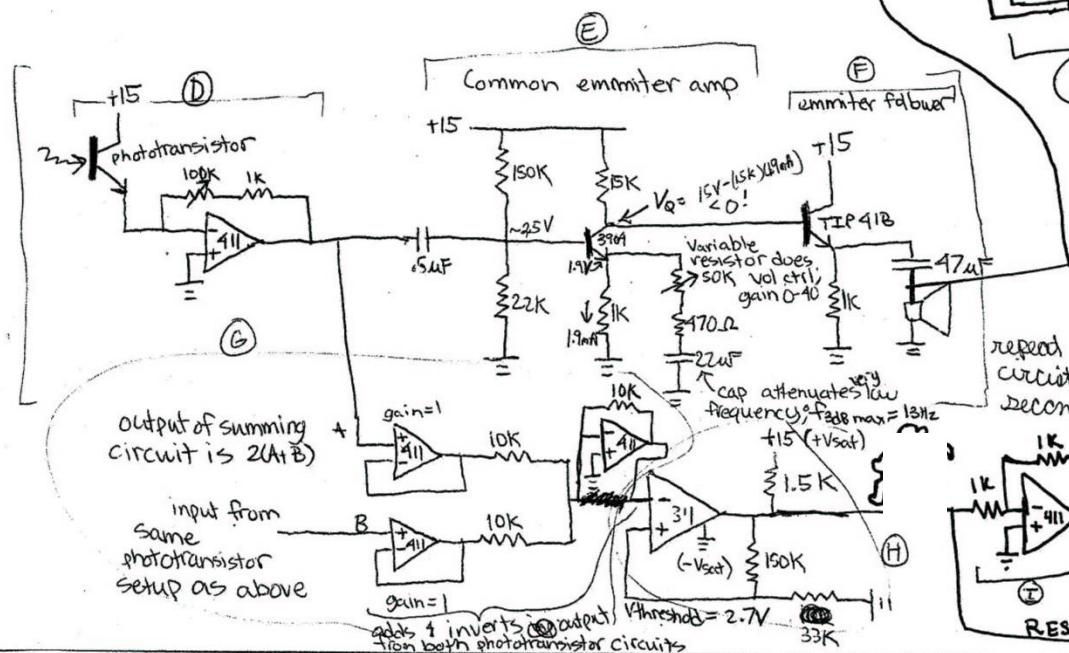

HELL CURRENT

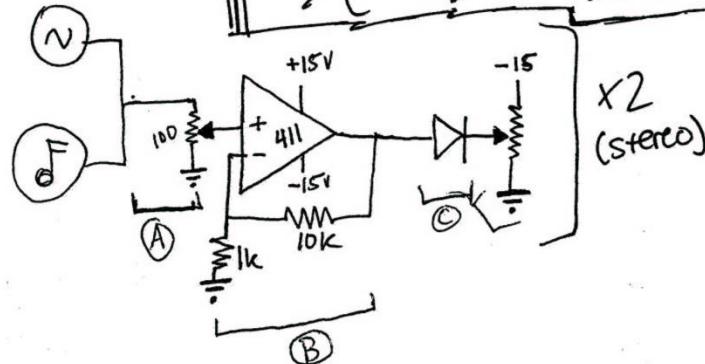

repeat this circuit for second speaker

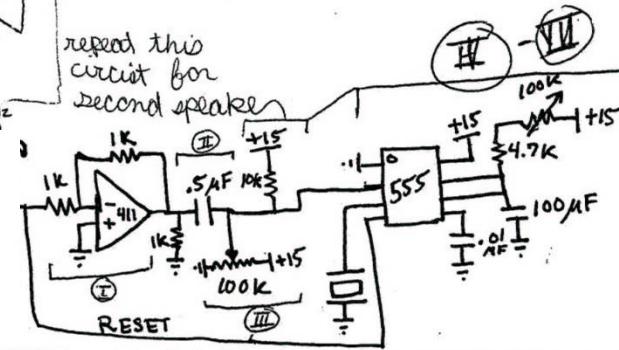

Output of summing circuit is $2(A+B)$

input from
same
phototransistor
setup as above

All the physics you Need To Know

All the physics you Need To Know

- Like charges repel,
opposites attract

Ohm's 3 Laws

(from U.S. Army Manual)

Ohm's 3 Laws

(from U.S. Army Manual)

- $V = IR$

Ohm's 3 Laws

(from U.S. Army Manual)

- $V = IR$
- $I = V / R$

Ohm's 3 Laws

(from U.S. Army Manual)

- $V = IR$
- $I = V / R$
- $R = V / I$

Ohm's 3 Laws

(from U.S. Army Manual)

- $V = IR$
- $I = V / R$
- $R = V / I$

Ohm's 3 Laws

(from U.S. Army Manual)

- $I = V / Z$ (impedance)

- $V = IR$

- $I = V / R$

- $R = V / I$

Beatles or Stones?

- A Beatles
- B Stones
- C who cares?
- D 42

Voltage Divider

IF

$$V_{in} = 10 \text{ V}$$

$$R_1 = 4\text{k} \quad R_2 = 6\text{k}$$


Then

A. $V_{out} = 4\text{V}$

B. $V_{out} = 1.67\text{V}$

C. $V_{out} = 6\text{V}$

D. $V_{out} = 2.5\text{V}$

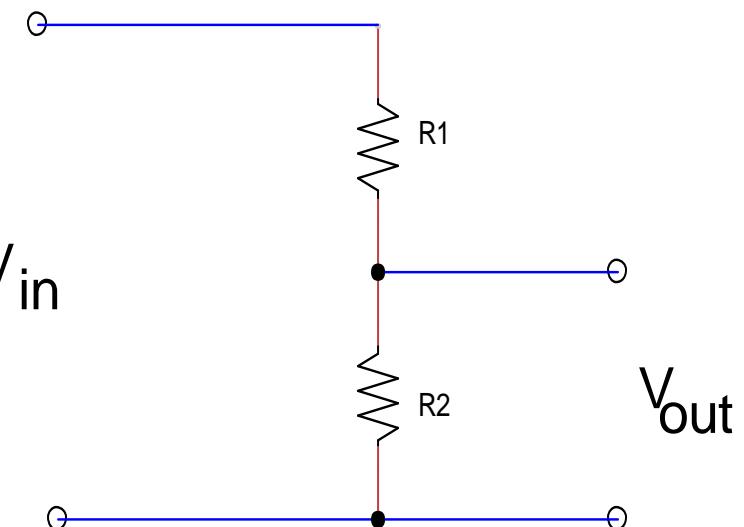

Voltage Divider

IF

$$V_{in} = 10 \text{ V}$$

$$R_1 = 4\text{k} \quad R_2 = 6\text{k}$$


Then

A. $V_{out} = 4\text{V}$

B. $V_{out} = 1.67\text{V}$

C. **$V_{out} = 6\text{V}$**

D. $V_{out} = 2.5\text{V}$

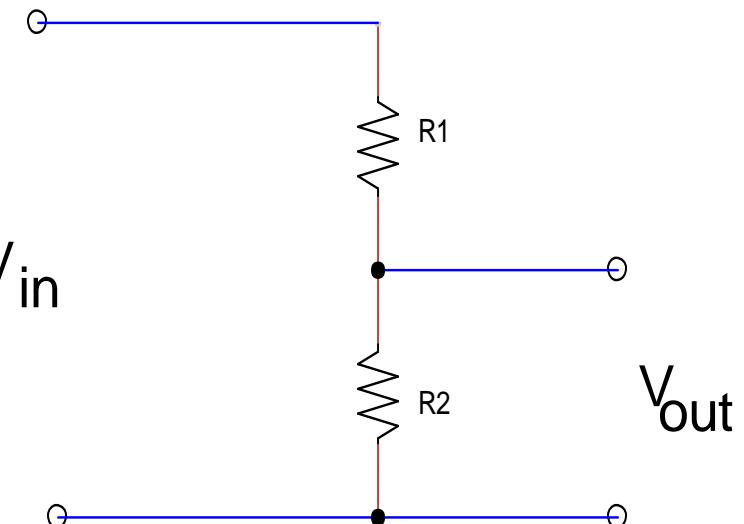




Voltage Divider

A. $V_{out} = V_{in} * R_2 / (R_1 + R_2)$

B. $V_{out} = V_{in} * (R_1 + R_2) / R_1$

C. $V_{out} = V_{in} * R_1 / (R_1 + R_2)$

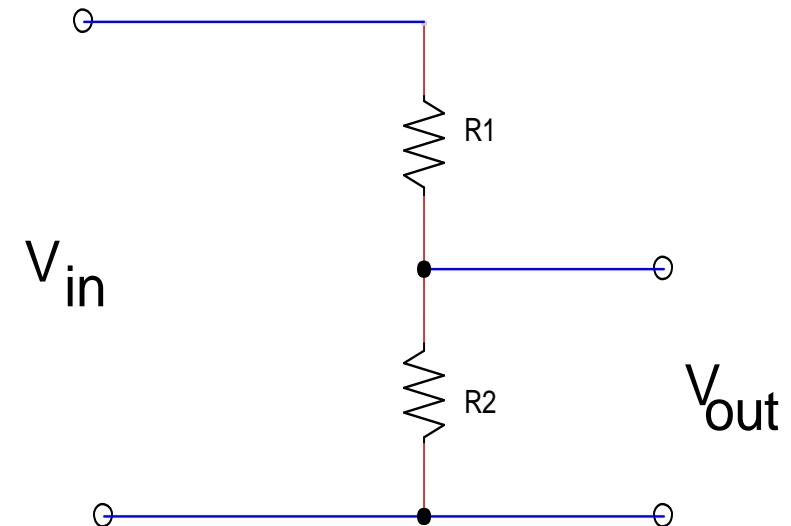D. $V_{out} = V_{in} * (R_1 + R_2) / R_2$




Voltage Divider

A. $V_{out} = V_{in} * R_2/(R_1 + R_2)$

B. $V_{out} = V_{in} * (R_1+R_2)/R_1$

C. $V_{out} = V_{in} * R_1/(R_1+R_2)$

D. $V_{out} = V_{in} * (R_1+R_2)/R_2$

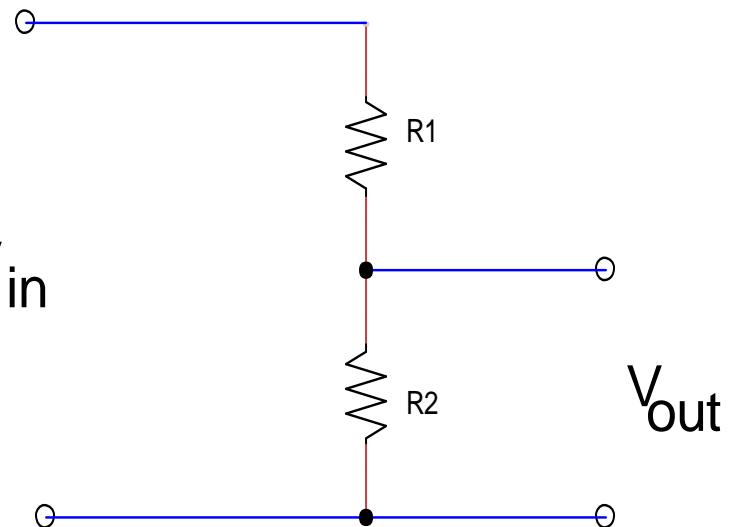

Current Divider

- What is I_1 , the current through R_1 ?

- A

$$I_1 = I_{in} \frac{R_2}{R_1 + R_2}$$

- B


$$I_1 = I_{in} \frac{R_2}{R_1}$$

- C

$$I_1 = I_{in} \frac{R_1 + R_2}{R_2}$$

- D


$$I_1 = I_{in} \frac{R_1}{R_1 + R_2}$$

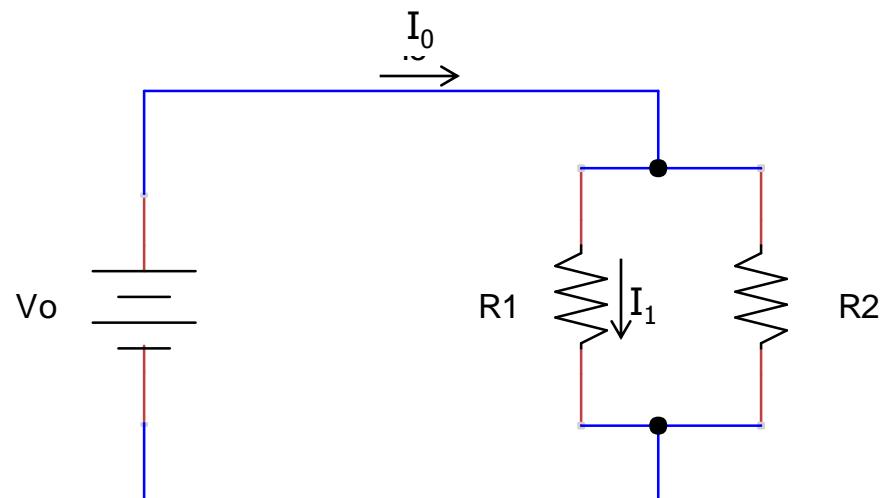

Current Divider

What is I_o ?


- A. 1 mA
- B. 2 mA
- C. 4 mA
- D. 8 mA

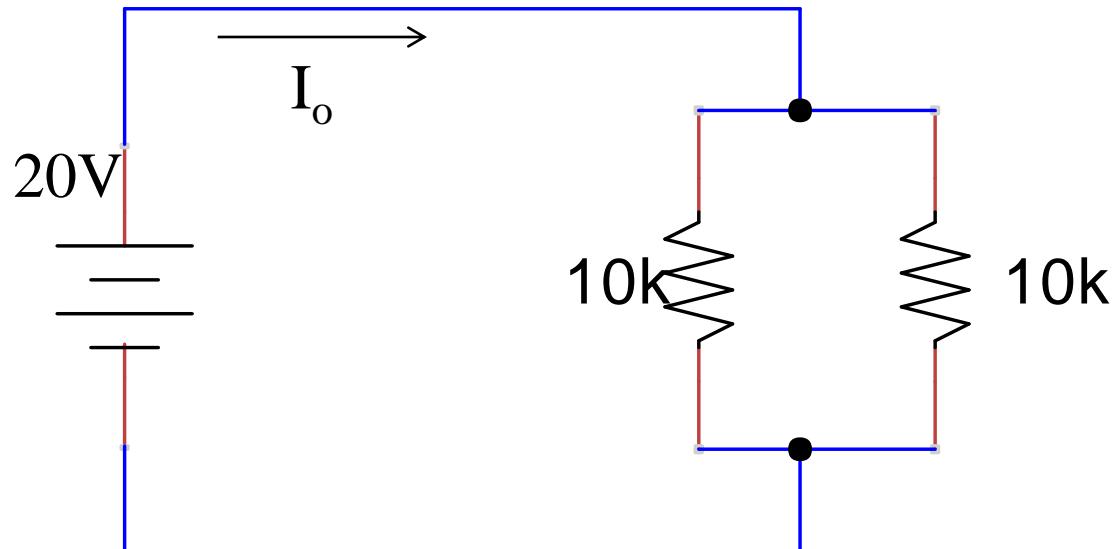

Current Divider

What is I_o ?


- A. 1 mA
- B. 2 mA
- C. 4 mA
- D. 8 mA

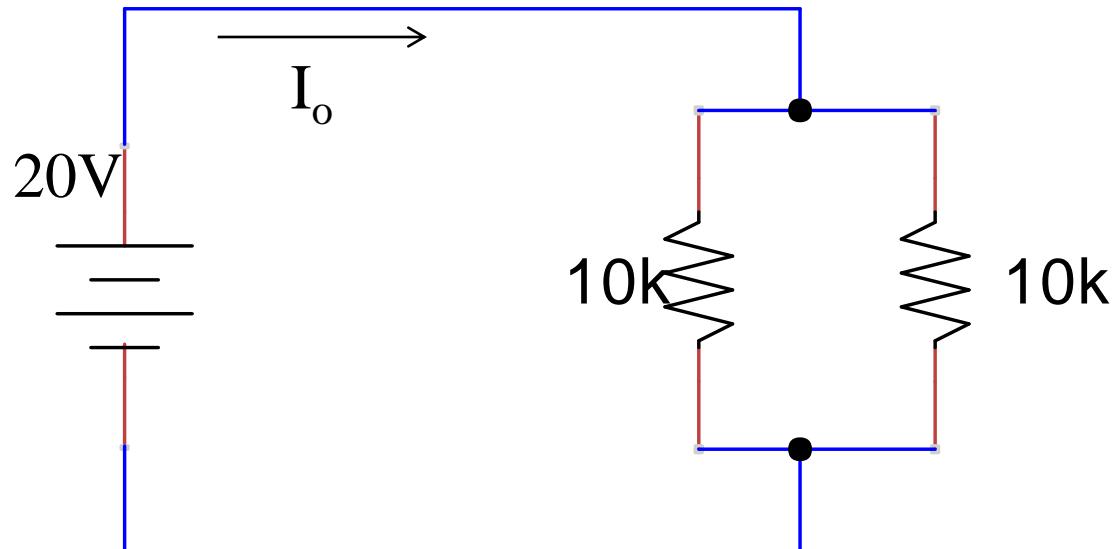

Current Divider

**One of the resistors is changed to 5k.
Which is true
about I_o ?**

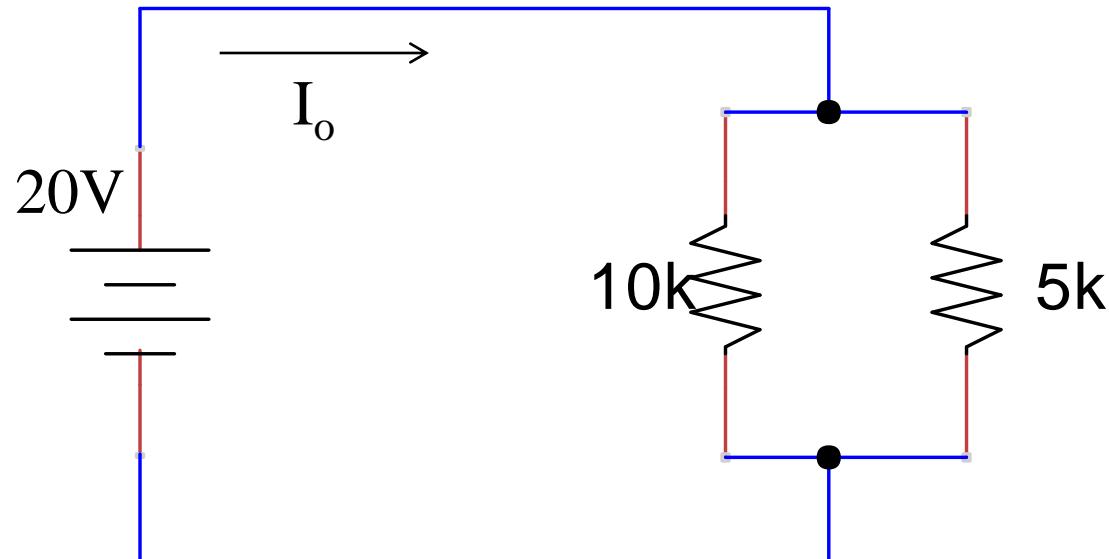
- A. I_o decreases
- B. I_o increases
- C. I_o stays the same



Current Divider


**One of the resistors is changed to 5k.
Which is true
about I_o ?**

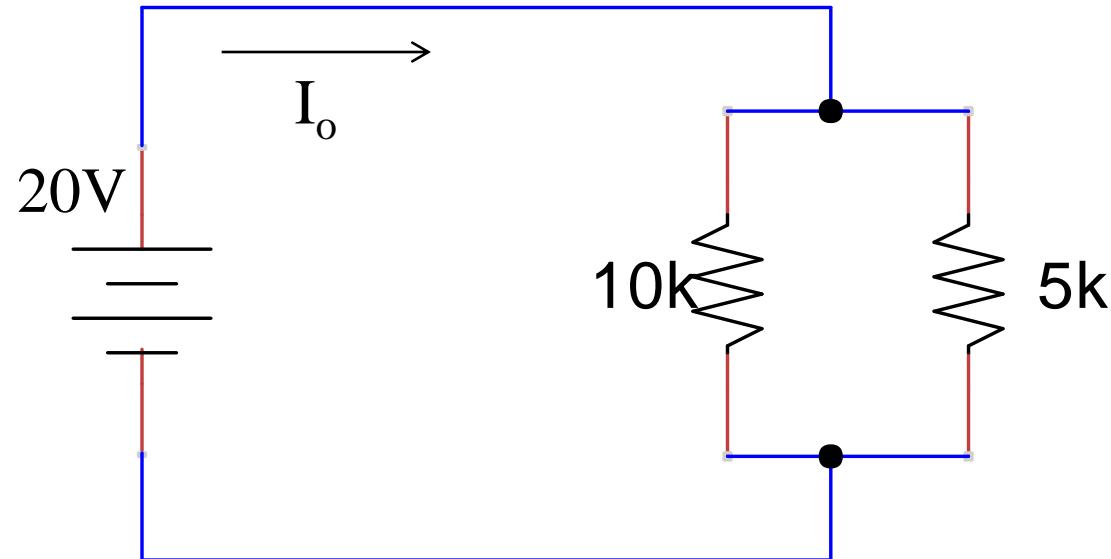- A. I_o decreases
- B. I_o increases
- C. I_o stays the same



Current Divider

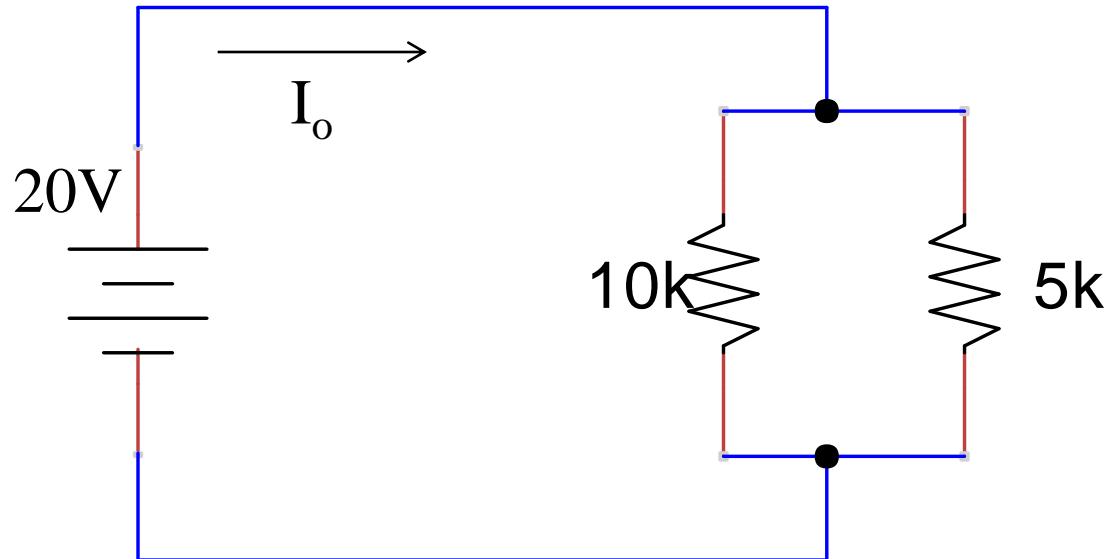
Which carries more current: the 10k or 5k resistor?



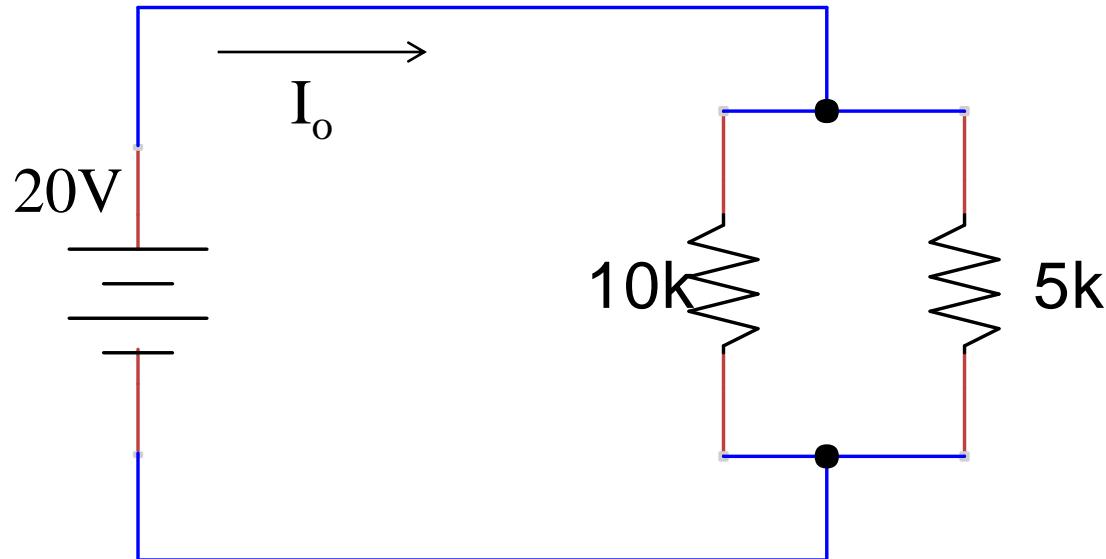- A. 10k
- B. 5k
- C. Same current

Current Divider

Which carries more current: the 10k or 5k resistor?



- A. 10k
- B. 5k
- C. Same current


Current Divider

Now, how much current in the 10k resistor?

A. 0

B. 2mA

C. ∞

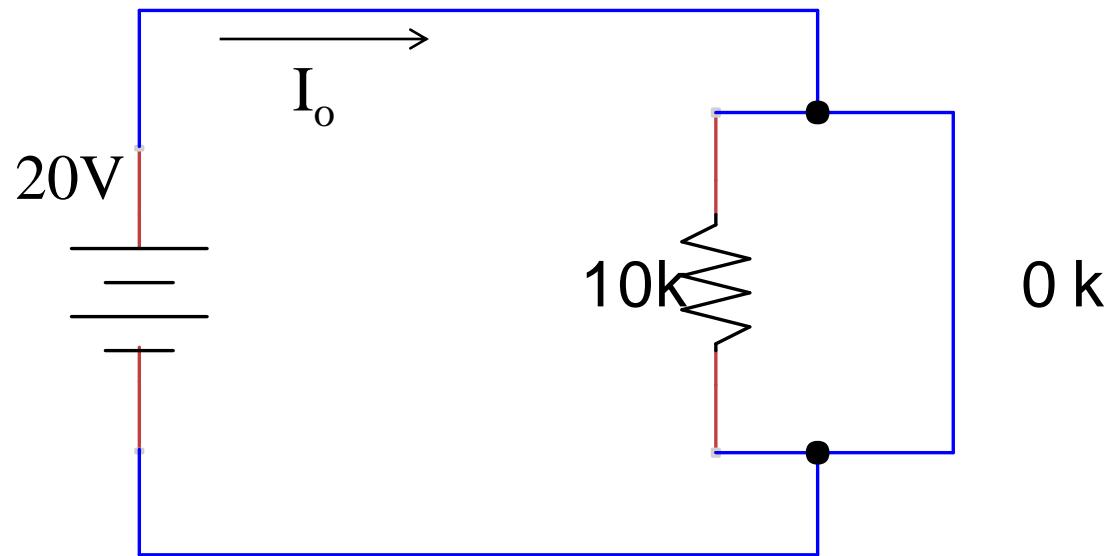


Current Divider

Now, how much current in the 10k resistor?

A. 0

B. 2mA

C. ∞

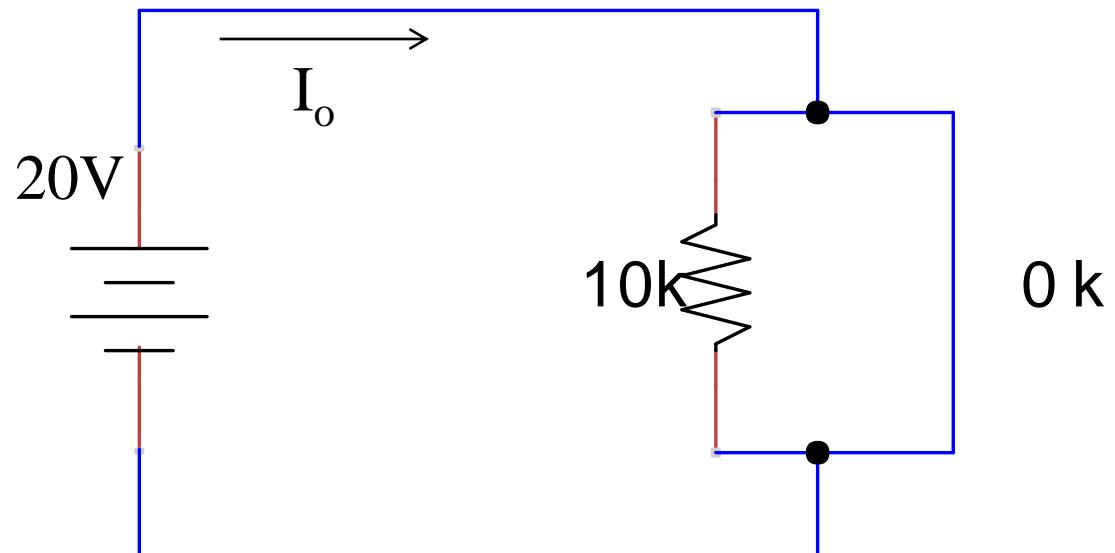

Current Divider


What is I_o ?

A. 0

B. 2mA

C. ∞


D. Cannot be determined

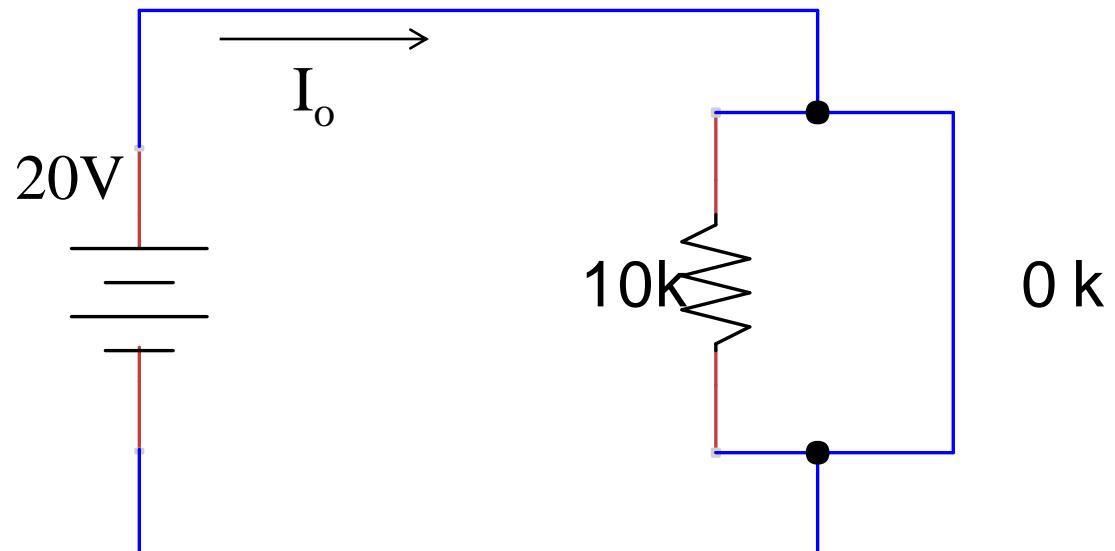

Current Divider

What is I_o ?

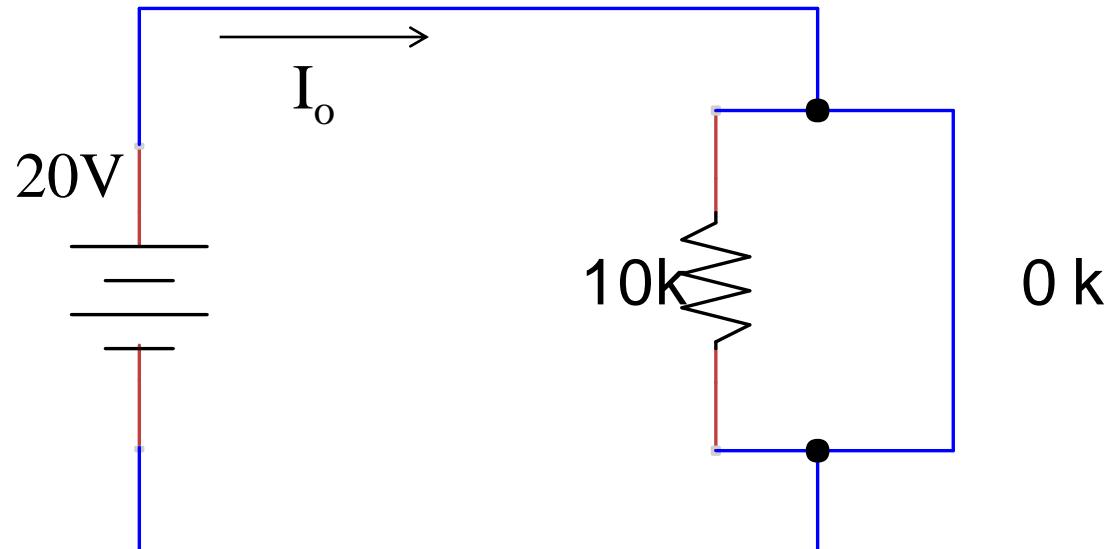- A. 0
- B. 2mA
- C. ∞
- D. Cannot be determined






Thevenin

Short Circuit Current

$$I_{sc} = ?$$

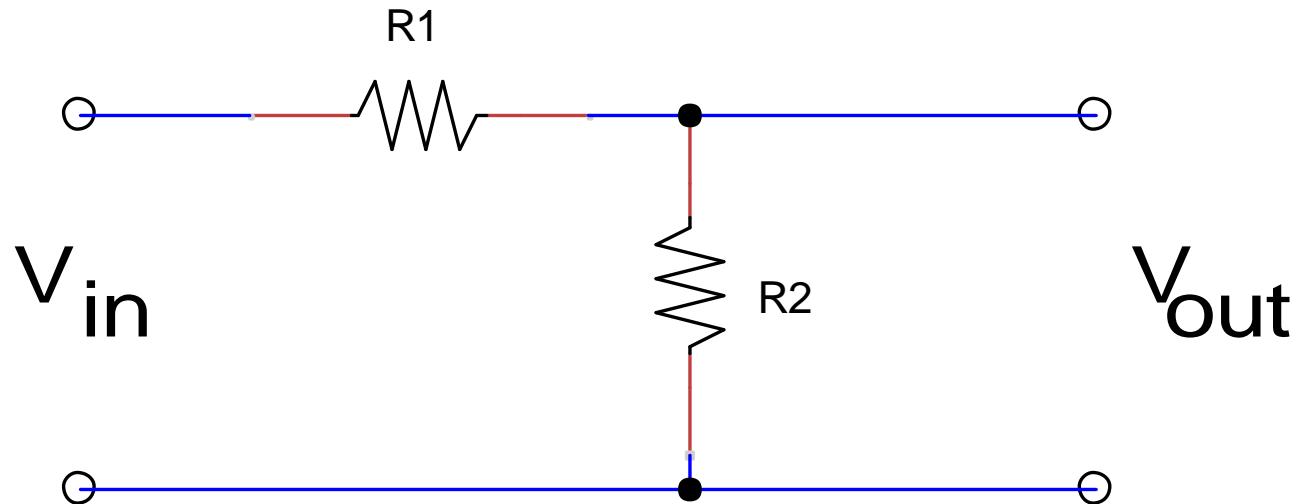


- A. $V_{in} / (R_2 + R_1)$
- B. V_{in} / R_2
- C. $V_{in} * R_1$
- D. V_{in} / R_1

Thevenin

Short Circuit Current


$$I_{sc} = ?$$

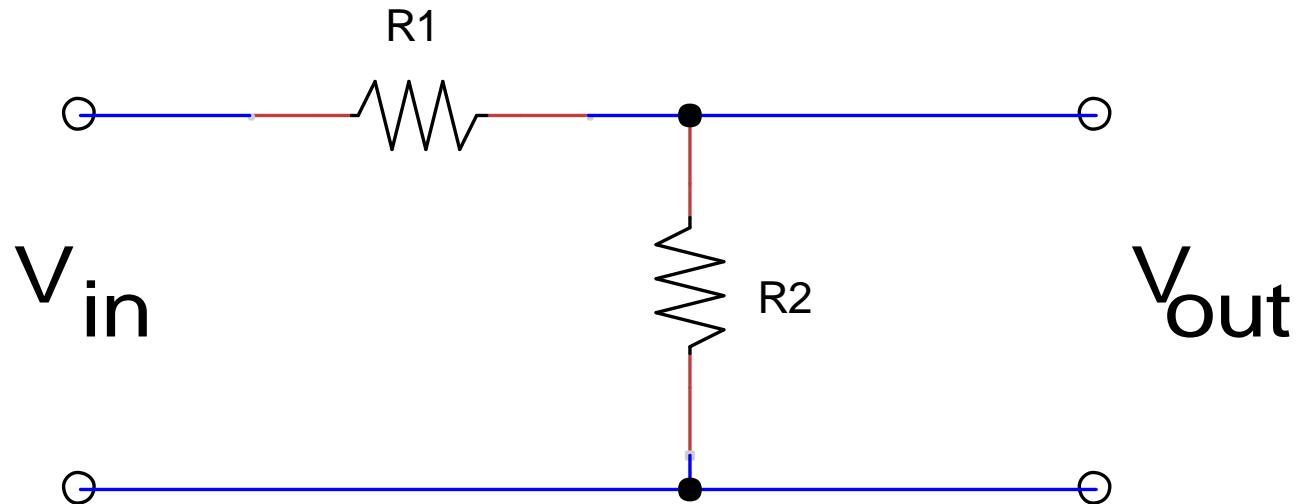

- A. $V_{in} / (R_2 + R_1)$
- B. V_{in} / R_2
- C. $V_{in} * R_1$
- D. V_{in} / R_1

Thevenin

Open Circuit Voltage

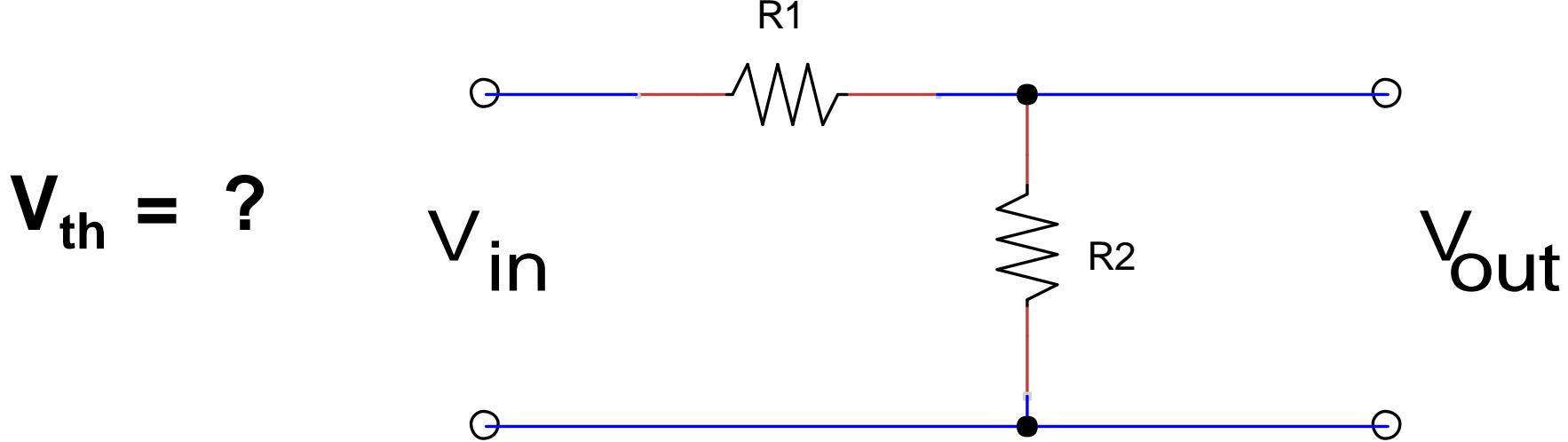


$$V_{th} = ?$$

- A. $V_{in} / (R_2 + R_1)$
- B. $V_{in} * R_1 / (R_1 + R_2)$
- C. $V_{in} * R_2 / R_1$
- D. $V_{in} * R_2 / (R_1 + R_2)$

Thevenin

Open Circuit Voltage

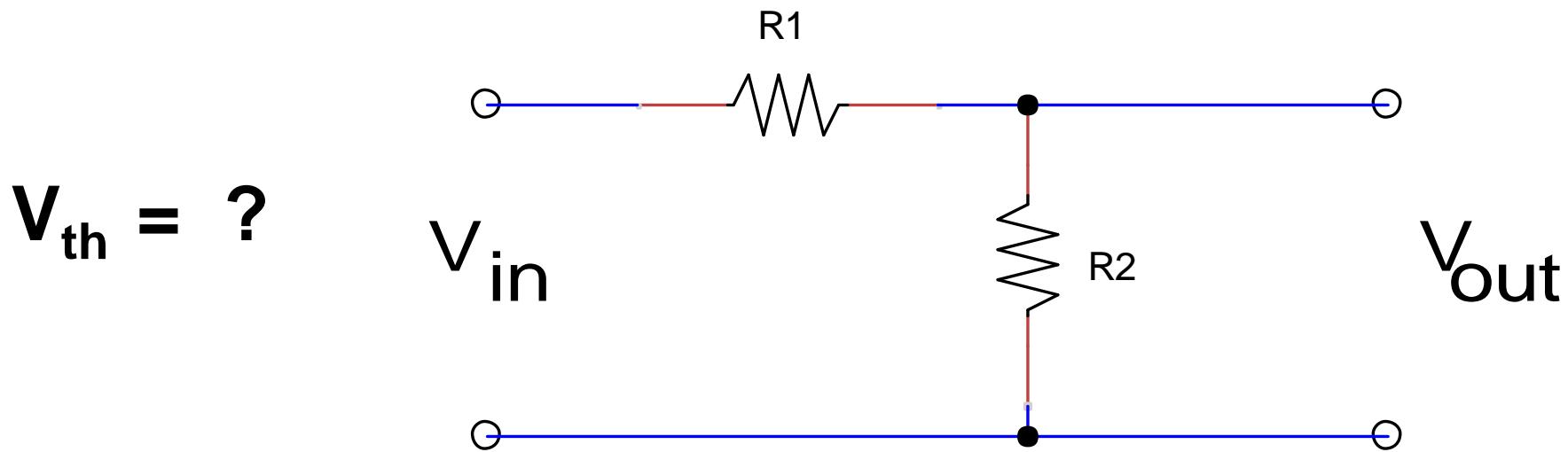

$$V_{th} = ?$$

A. $V_{in} / (R_2 + R_1)$

B. $V_{in} * R_1 / (R_1 + R_2)$

C. $V_{in} * R_2 / R_1$

D. $\text{Vin} * \text{R2}/(\text{R1+R2})$