

U. Tietze · Ch. Schenk

Electronic Circuits

Design and Applications

With the Assistance of
E. Schmid

With 1168 Figures

Springer-Verlag Berlin Heidelberg New York
London Paris Tokyo Hong Kong Barcelona

2 Passive RC and LRC networks

RC networks are of fundamental importance to circuit design. As their effect is the same in all circuits, their operation will be described in some detail.

2.1 The lowpass filter

A lowpass filter is a circuit which passes low-frequency signals unchanged and attenuates at high frequencies, introducing a phase lag. Figure 2.1 shows the simplest type of RC lowpass filter circuit.

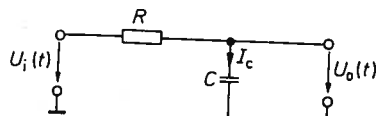


Fig. 2.1 Simple lowpass filter

2.1.1 Frequency-domain analysis

To calculate the frequency response of the circuit, we use the voltage divider formula, written in complex notation as:

$$\underline{A}(j\omega) = \frac{U_o}{U_i} = \frac{1/j\omega C}{R + 1/j\omega C} = \frac{1}{1 + j\omega RC} \quad (2.1)$$

Factoring according to

$$\underline{A} = |\underline{A}| e^{j\varphi}$$

we obtain the frequency response of the absolute value or magnitude and of the phase shift:

$$|\underline{A}| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}, \quad \varphi = -\arctan \omega RC \quad (2.2)$$

The two curves are shown in Fig. 2.2.

To calculate the 3 dB cutoff frequency f_c , we substitute

$$|\underline{A}| = \frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + \omega_c^2 R^2 C^2}}$$

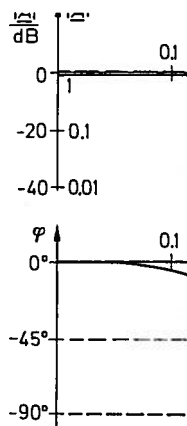


Fig. 2.2

into Eq. (2.2), which gives

From Eq. (2.2), the phase shift can be easily constructed using

- 1) At low frequencies $f \ll f_c$
- 2) At high frequencies $f \gg f_c$ inversely proportional to f by a factor of 10, the gain decreases by 20 dB/decade or 6 dB/octave
- 3) At $f = f_c$, $|\underline{A}| = 1/\sqrt{2} \approx 0.707$

2.1.2

In order to analyze the circuit voltage to the input, as shown in Fig. 2.1, we apply Kirchhoff's current law at the node between the resistor and the capacitor.

With $I_C = C \dot{U}_o$, we obtain the

$$RC \dot{U}_o + U_o = U_i$$

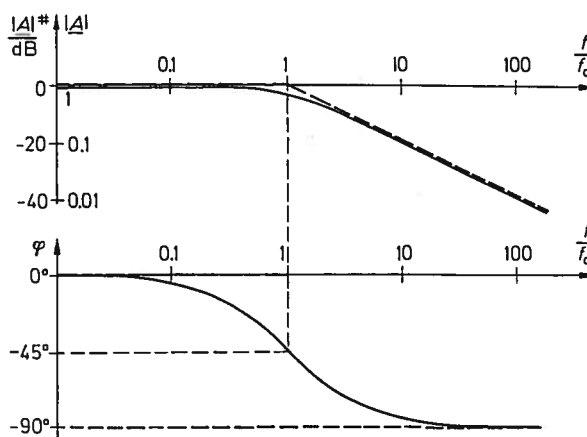


Fig. 2.2 Bode plot of a lowpass filter

into Eq. (2.2), which gives

$$f_c = \frac{1}{2\pi} \omega_c = \frac{1}{2\pi RC} \quad (2.3)$$

From Eq. (2.2), the phase shift at this frequency is $\varphi = -45^\circ$.

As we can see from Fig. 2.2, the amplitude-frequency response $|A| = \hat{U}_o/\hat{U}_i$ can be easily constructed using the two asymptotes:

- 1) At low frequencies $f \ll f_c$, $|A| = 1 \approx 0$ dB.
- 2) At high frequencies $f \gg f_c$, from Eq. (2.2) $|A| \approx 1/\omega RC$, i.e. the gain is inversely proportional to the frequency. When the frequency is increased by a factor of 10, the gain is reduced by the same factor, i.e. it decreases by 20 dB/decade or 6 dB/octave.
- 3) At $f = f_c$, $|A| = 1/\sqrt{2} \approx -3$ dB.

2.1.2 Time-domain analysis

In order to analyze the circuit in the time domain, we apply a step function of voltage to the input, as shown in Fig. 2.3. To calculate the output voltage, we apply Kirchhoff's current law to the (unloaded) output and obtain in accordance with Fig. 2.1

$$\frac{U_i - U_o}{R} - I_C = 0.$$

With $I_C = C\dot{U}_o$, we obtain the differential equation

$$RC\dot{U}_o + U_o = U_i = \begin{cases} U_r & \text{for } t > 0 \text{ in Case a,} \\ 0 & \text{for } t > 0 \text{ in Case b.} \end{cases} \quad (2.4)$$

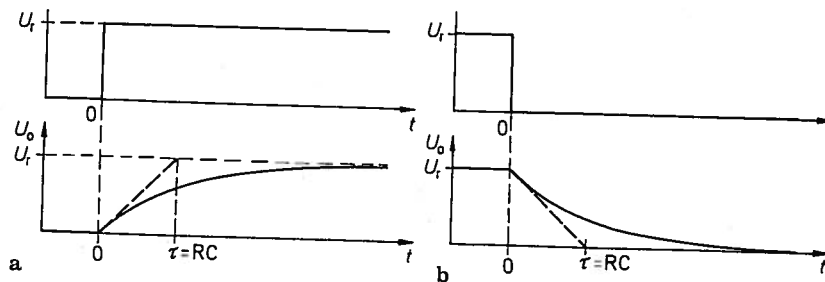


Fig. 2.3 a and b Step-response of a lowpass filter

It has the following solutions:

Case a:

$$U_o(t) = U_r(1 - e^{-\frac{t}{RC}});$$

Case b:

$$U_o(t) = U_r e^{-\frac{t}{RC}}. \quad (2.5)$$

This curve is also plotted in Fig. 2.3. We can see that the steady-state values $U_o = U_r$ or $U_o = 0$ are only attained asymptotically. As a measure of the response time, a *time constant* τ is therefore defined. This indicates how long it takes for the deviation from the steady-state value to equal $1/e$ times the step

Response accuracy	37%	10%	1%	0.1%
Response time	τ	2.3τ	4.6τ	6.9τ

Fig. 2.4 Response time of a lowpass filter

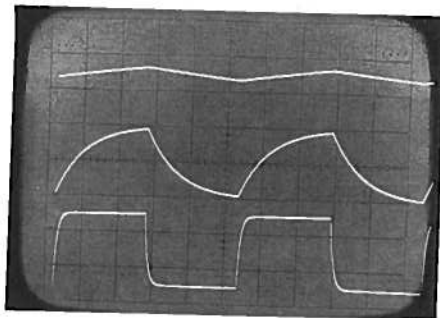


Fig. 2.5 Square-wave response of a lowpass filter for various frequencies

Upper curve: $f_i = 10 f_c$

Middle curve: $f_i = f_c$

Lower curve: $f_i = \frac{1}{10} f_c$

The response time for small signals is given in Figure 2.4 lists a number of

If a square-wave voltage function is truncated after a certain time, the output of a lowpass filter is obtained at the output of the filter. This characteristic is

Lowpass filter

In the previous section, we compared the input and output of a lowpass filter. The output of the filter is inferred directly from differential equations.

Lowpass filter

For unsymmetrical alternating signals, the Fourier expansion is not satisfied. The Fourier expansion is the arithmetic mean

where T is the period of the signal. The Fourier series are combined to form a single curve that corresponds to that of the input signal. That its arithmetic mean is zero is the form

For voltage $U_i(t)$, the concentration of the DC component is transferred to the output

U_o

If the time constant $\tau = RC$

magnitude. From Eq. (2.5) the time constant is

$$\tau = RC . \quad (2.6)$$

The response time for smaller deviations can also be derived from Eq. (2.5). Figure 2.4 lists a number of important parameters.

If a square-wave voltage of period T is applied as the input signal, the e -function is truncated after time $T/2$ by the subsequent step. Which final value is obtained at the output depends on the ratio between the time $T/2$ and the time constant τ . This characteristic is clearly illustrated by the oscillogram in Fig. 2.5.

Lowpass filter as an integrating circuit

In the previous section we saw that the alternating output voltage is small compared with the input voltage if a signal frequency $f \gg f_c$ is selected. The lowpass filter operates then as an integrating circuit. This property can be inferred directly from differential Eq. (2.4). Assuming that $|U_o| \ll |U_i|$, it follows that

$$RC \dot{U}_o = U_i ,$$

$$U_o = \frac{1}{RC} \int_0^t U_i(\tilde{t}) d\tilde{t} + U_o(0) .$$

Lowpass filter as an averaging circuit

For unsymmetrical alternating voltages, the above condition $f \gg f_c$ is not satisfied. The Fourier expansion in fact contains a constant which is identical to the *arithmetic mean*

$$\bar{U}_i = \frac{1}{T} \int_0^T U_i(t) dt$$

where T is the period of the input voltage. If all the higher-order terms of the Fourier series are combined, a voltage $U'_i(t)$ is obtained whose characteristic corresponds to that of the input voltage, but which is displaced from zero such that its arithmetic mean is zero. The input voltage may therefore be expressed in the form


$$U_i(t) = \bar{U}_i + U'_i(t) .$$

For voltage $U'_i(t)$, the condition $f \gg f_c$ can be satisfied; it is integrated, whereas the DC component is transferred linearly. The output voltage therefore becomes

$$U_o = \underbrace{\frac{1}{RC} \int_0^t U'_i(\tilde{t}) d\tilde{t}}_{\text{residual ripple}} + \underbrace{\bar{U}_i}_{\text{mean value}} . \quad (2.7)$$

If the time constant $\tau = RC$ is made sufficiently large, the ripple is insignificant

ks

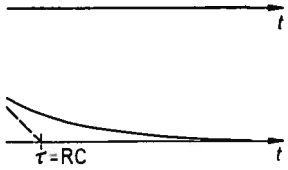

lowpass filter

Case b:

$$U_o(t) = U_i e^{-\frac{t}{RC}} . \quad (2.5)$$

that the steady-state values are equal. As a measure of the time constant τ , it indicates how long it takes for the output to equal $1/e$ times the step input.

%	0.1%
0.6τ	6.9τ

lowpass filter



for various frequencies

re
ce
re
ce

$$U_o \approx \bar{U}_i . \quad (2.8)$$

2.1.3 Rise time and cutoff frequency

Another parameter for characterizing lowpass filters is the rise time t_r . This denotes the time taken for the output voltage to rise from 10 to 90% of the final value when a step is applied to the input. From the e-function in Eq. (2.5) we obtain

$$t_r = t_{90\%} - t_{10\%} = \tau(\ln 0.9 - \ln 0.1) = \tau \ln 9 \approx 2.2\tau .$$

Consequently, with $f_c = 1/2\pi\tau$

$$\boxed{t_r \approx \frac{1}{3f_c}} . \quad (2.9)$$

In approximation this relation is also true for higher-order lowpass filters.

If a number of lowpass filters with various rise times t_{ri} are connected in series, the resultant rise time is

$$t_r \approx \sqrt{\sum_i t_{ri}^2} , \quad (2.10)$$

and the cutoff frequency is

$$f_c \approx \left(\sum_i f_{ci}^{-2} \right)^{-\frac{1}{2}} .$$

Hence, for n lowpass filters having the same cutoff frequency

$$\boxed{f_c \approx \frac{f_{ci}}{\sqrt{n}}} . \quad (2.11)$$

2.2 The highpass filter

A highpass filter is a circuit which passes high-frequency signals unchanged and attenuates at low frequencies, introducing a phase lead. Figure 2.6 shows the simplest form of RC highpass filter circuit. The frequency response of the gain and phase shift is again obtained from the voltage divider formula:

$$\underline{A}(j\omega) = \frac{\underline{U}_o}{\underline{U}_i} = \frac{R}{R + 1/j\omega C} = \frac{1}{1 + 1/j\omega RC} . \quad (2.12)$$

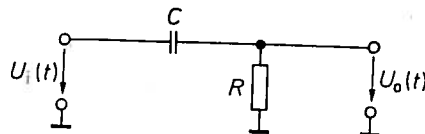


Fig. 2.6 Simple highpass filter

The two
the lowp

At this fi

As in
easily pl

1) A

2) A

pi

+

3) F.

To c
(unload

With \dot{U}_i

This yields

$$(2.8) \quad |A| = \frac{1}{\sqrt{1 + 1/\omega^2 R^2 C^2}} \quad \text{and} \quad \varphi = \arctan \frac{1}{\omega RC} . \quad (2.13)$$

The two curves are shown in Fig. 2.7. For the cutoff frequency, we obtain as with the lowpass filter:

$$f_c = \frac{1}{2\pi RC} . \quad (2.14)$$

At this frequency the phase shift is $+45^\circ$.

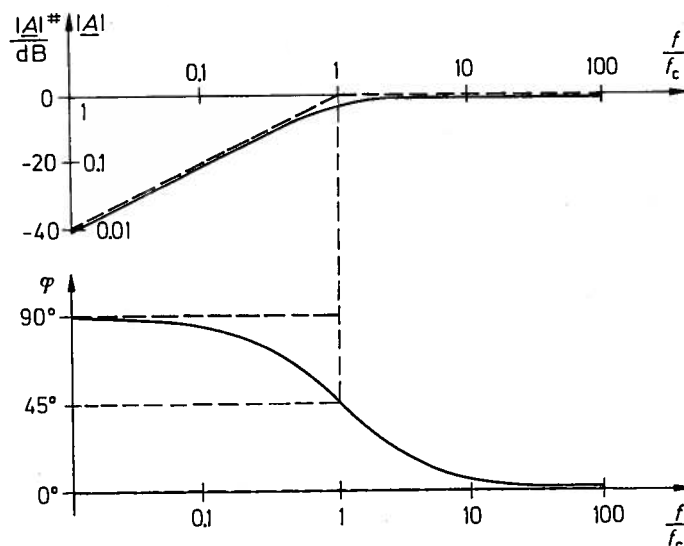


Fig. 2.7 Bode plot of a highpass filter

As in the case of the lowpass filter, the amplitude-frequency response can be easily plotted on a double-logarithmic scale using the asymptotes:

- 1) At high frequencies $f \gg f_c$, $|A| = 1 \cong 0$ dB.
- 2) At low frequencies $f \ll f_c$, from Eq. (2.13) $|A| \approx \omega RC$, i.e. the gain is proportional to the frequency. The slope of the asymptote is therefore +20 dB/decade or +6 dB/octave.
- 3) For $f = f_c$, $|A| = 1/\sqrt{2} \cong -3$ dB, as with the lowpass filter.

To calculate the step response, we apply Kirchhoff's current law to the (unloaded) output:

$$C \cdot \frac{d}{dt} (U_i - U_o) - \frac{U_o}{R} = 0 . \quad (2.15)$$

With $\dot{U}_i = 0$, this yields the differential equation

$$RC \dot{U}_o + U_o = 0 \quad (2.16)$$

$$U_o(t) = U_{o0} e^{-t/RC} \quad (2.17)$$

The time constant is therefore $\tau = RC$, as in the case of the lowpass filter.

In order to determine the initial value $U_{o0} = U_o(t=0)$, we have to consider that at the instant when the input voltage changes abruptly, the capacitor charge remains unchanged. The capacitor therefore acts as a voltage source of value $U = Q/C$. The output voltage accordingly shows the same step ΔU as the input voltage. If U_i goes from zero to U_r , the output voltage likewise jumps from zero to U_r (see Fig. 2.8a) then decays exponentially to zero again in accordance with Eq. (2.17).

If the input voltage now goes abruptly from U_r to zero, U_o jumps from zero to $-U_r$ (see Fig. 2.8b). Note that the output voltage assumes negative values even though the input voltage is always positive. This distinctive characteristic is frequently used in circuit design.

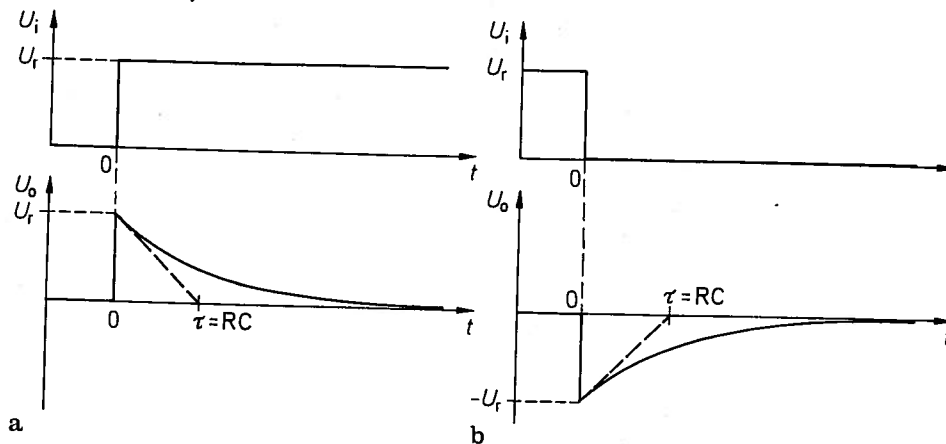


Fig. 2.8 a and b Step response of a highpass filter

Use as an RC coupling network

If a square-wave voltage periodic in $T \ll \tau$ is applied to the input, the capacitor charge barely changes during one half-cycle; the output voltage is identical to the input voltage apart from an additive constant. As no direct current can flow via the capacitor, the arithmetic mean of the output voltage is zero. No DC component of the input voltage is therefore transferred. It is this property which enables a highpass filter to be used as an *RC coupling network*.

Use as a differentiating circuit

If input voltages with frequencies $f \ll f_c$ are applied, $|U_o| \ll |U_i|$. Consequently, from differential Eq. (2.15)

$$U_o = RC \frac{dU_i}{dt}$$

Low-frequency input voltages are therefore differentiated.

The o
filter.

If a n
frequency

Conseque

It is fr
making it
divider, th
in that the
value.

Anoth
to compen
 C_k in Fig
capacitive
divider. C
frequencie

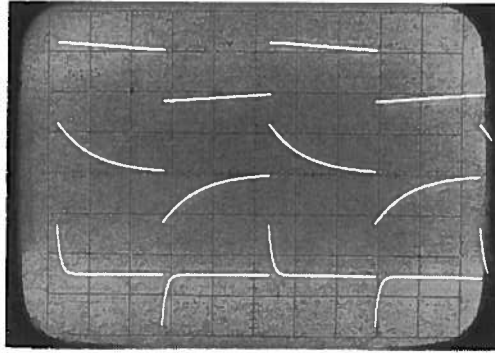


Fig. 2.9 Square-wave response of a highpass filter for various frequencies

Upper curve: $f_i = 10f_c$
 Middle curve: $f_i = f_c$
 Lower curve: $f_i = \frac{1}{10}f_c$

The oscillograms in Fig. 2.9 summarize the transient response of a highpass filter.

Series connection of several highpass filters

If a number of highpass filters are connected in series, the resultant cutoff frequency is

$$f_c \approx \sqrt{\sum_i f_{ci}^2} \quad (2.18)$$

Consequently, for n highpass filters having identical cutoff frequencies

$$f_c \approx f_{ci} \cdot \sqrt{n} \quad (2.19)$$

2.3 Compensated voltage divider

It is frequently the case that a resistive voltage divider is capacitively loaded, making it a lowpass filter. The lower the resistance selected for the voltage divider, the higher the cutoff frequency of the filter. However, limits are imposed in that the input resistance of the divider should not be reduced below a specified value.

Another possible way of raising the cutoff frequency is to use a highpass filter to compensate for the effect of the lowpass filter. This is the purpose of capacitor C_k in Fig. 2.10. It is dimensioned such that the resultant parallel-connected capacitive voltage divider has the same division ratio as the resistive voltage divider. Consequently, the same voltage division is produced at high and low frequencies. This means that

$$\frac{C_k}{C_L} = \frac{R_2}{R_1}$$