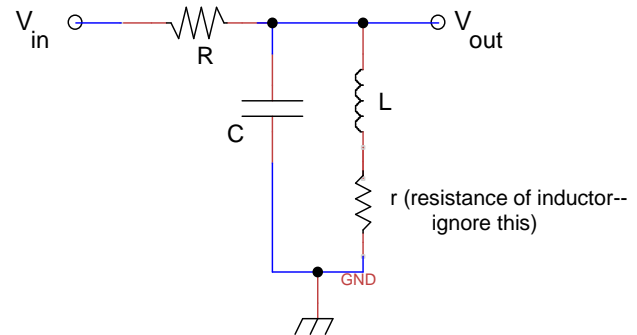


## RLC Resonance – Bandpass Filter

You will drive this circuit with a sine wave.

1. Measure the attenuation (dB) and phase shift vs. frequency (Hz) for the RLC this circuit: Use these values:  
 $R = 100k$ ,  $C = .01 \text{ uF}$ ,  $L = 10mH$   
 Take sufficient data to generate a pair of Bode plots (magnitude and phase) vs frequency
2. Make the Bode plots and see if you can figure out: what is this filter doing?
3. Determine the  $Q$  of the circuit from the magnitude plot,  
 $Q \equiv (f_0 / \Delta f_{3dB})$ .
4. Change  $R$  to 100 ohm, and do another Bode plot, this time for magnitude only. What happened to the  $Q$ ?
5. Return to  $R = 100k$ , change  $L$  to 1 mH,  $C$  to 0.1 uF. Repeat #4.



Explain these results using the transfer function derived in class:

$$H(\omega) = \frac{V_{out}}{V_{in}} = \left[ 1 + iR \left( \omega C - \frac{1}{\omega L} \right) \right]^{-1}$$

### BONUS:

It is claimed that a square wave can be constructed from this infinite Fourier series:

$$V_{square} \sim \sin(\omega t) + \frac{1}{3}\sin(3\omega t) + \frac{1}{5}\sin(5\omega t) + \frac{1}{7}\sin(7\omega t) \dots$$

Return the circuit to the original values of  $R$ ,  $L$   $C$ .

Measure these Fourier coefficients as follows:

Drive the circuit with a *square* wave,. Start with the resonant frequency you measured in Part 1 above. Measure the amplitude of the peak of the wave. Then reduce the frequency to 1/3, measure the amplitude of the peak of the wave.

See how many Fourier coefficients you can measure

### HOMEWORK:

Derive this expression for the  $Q$  of the circuit and see if your results match this:

$$Q = R\sqrt{C/L}$$